 


## ELE504E MIDTERM EXAM

Name:

Number:

**Q1)** The Layout of a complex gate is shown. The gate has five inputs (from left to right: X1, X2, X3, X4, X5), an output (OUT) and VDD and GND connections.



- Draw the electrical schematic of the gate.
- Find the Boolean expression realized by the gate.
- Write the netlist of the circuit assuming the gate is to be realized in TSMC 0.18 technology.


**Q2)** A chain of three inverters fabricated in TSMC 0.18 is to drive a capacitive load of 5pF.

- a)** Determine all device widths in the chain in such a way that total latency is minimized.


Inverter #	Wn	Wp
1	0.5u	
2		
3		

- b)** Calculate the total chain latency.
- c)** Verify the results using a SPICE simulation.

 **Q3)** You are supposed to implement the Boolean function  $Y = X_1 + X_2 + X_3$  with CMOS static gates. Since such gates inevitably invert, you have two options:



or

 

- a)** Assuming that all devices in all options are built with minimum geometry devices, which option will yield a shorter latency? Explain.
- b)** Verify the results found in (a) with a SPICE simulation. Write your input netlist and provide your simulation results.