

Implementing Boolean Functions by Using Zipper Logic

ELE504E - Homework 10, Spring 2025

1 Procedure

In this session, you are going to implement a Boolean function using Zipper Logic Gates.


- Fill in the truth table of Boolean Function :.....

A	B	C	D	Y


- Beginning with the Pull-down Network, draw the complete electrical schematic of 3-stage zipper gate whose stages are indicated as:

.....

3-stage Zipper Gate

 

- Write the spice netlist of your circuit above (including the inverters), with minimum-geometry devices (calculate ad, as, pd, ps of each device) and carefully indicate all variables at appropriate nodes.
- Define input signals A, B, C and C by using the following lines:
`va <input_node_a> 0 pulse 0 1.8 16.1n 100p 100p 15.9n 32n`
`vb <input_node_b> 0 pulse 0 1.8 8.1n 100p 100p 7.9n 16n`
`vc <input_node_c> 0 pulse 0 1.8 4.1n 100p 100p 3.9n 8n`
`vd <input_node_d> 0 pulse 0 1.8 2n 100p 100p 2n 4n`
- Define the clock signals ϕ and $\bar{\phi}$ from the timing diagram given below:

 

- Perform a transient analysis up to 31.5 ns with 10 ps timestep. Plot ϕ , $\bar{\phi}$, D, C, B, A and *out* with the following command:
`plot v(<input_node_phi>) v(<input_node_phin>) v(<input_node_d>)+2`
`v(<input_node_c>)+4 v(<input_node_b>)+6 v(<input_node_a>)+8`
`v(<output_node_out>)+10`