

Spice Homework #2

ELE504E, Spring 2025

1 DC Sweep

Figure 1.1 contains twelve resistors each having a value of “ R ” formed in a cube shape. Find the equivalent resistance:

- Between the points a-d.
- Between the points a-c.
- Between the points a-f.

in terms of “ R ”. For simulation, please follow the steps below:

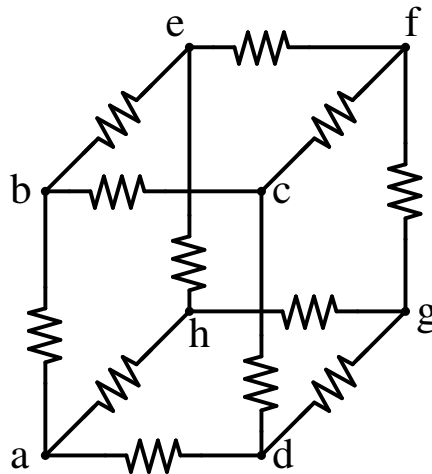


Figure 1.1. Resistor Cube.

- Select an appropriate resistor value (i.e. $R = 1k\Omega$).
- Write the netlist of the circuit in Figure 1.1.
- Define a DC voltage source between the points where the resistance is to be calculated.
- Place a wire (a zero-ohm resistor) from the minus terminal of the voltage source to the ground (node-0)
- Perform a DC-Sweep from 0.1V to 1V with 10mV steps.
- Plot the equivalent resistance by dividing the voltage between the terminals of the voltage source and the current drawn from the voltage source.
- Find the equivalent resistance in terms of “ R ”.

2 Transient Analysis

Find the time-constant of the RC circuit in Figure 2.1 in terms of parameters “ R ” & “ C ”. For simulation, please follow the steps below:

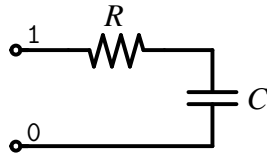


Figure 2.1. Simple RC Circuit.

- Select $R = 1k\Omega$ and $C = 1nF$.
- Write the netlist of the circuit in Figure 2.1.
- Define a pulse voltage source between the nodes 1 and 0 with the following parameters:
 - $V_1 = 0V$.
 - $V_2 = 1V$.
 - $T_D = 1\mu s$.
 - $T_R = 10n$.
 - $T_F = 10n$.
 - $PW = 5\mu s$.
 - $PER = 10\mu s$.
- Perform a transient Analysis with 10ns timesteps up to $20\mu s$.
- Plot the voltage across the capacitor and measure the time constant τ using Figure 2.2.
- Express τ in terms of parameters “ R ” & “ C ”

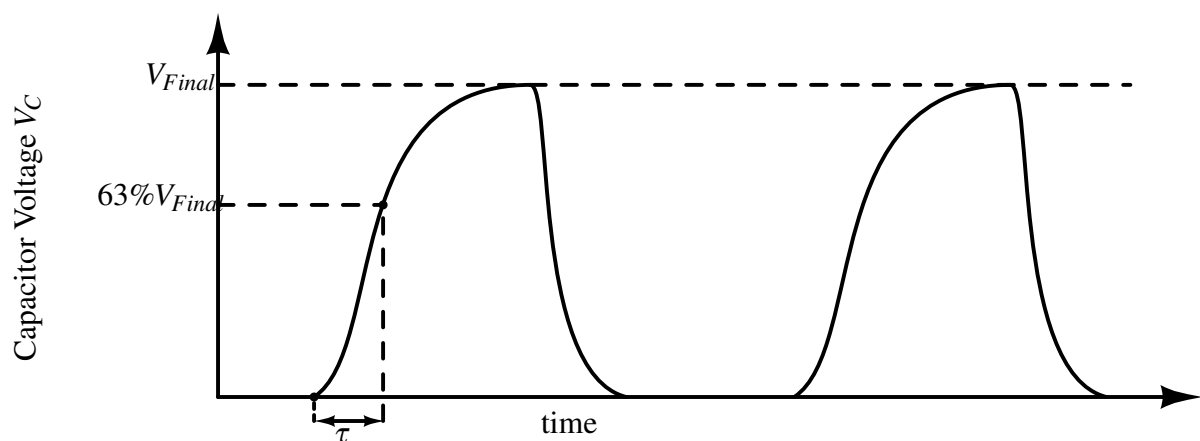


Figure 2.2. Measuring Time Constant “ τ ”.

Take 2 screenshots (one for DC Sweep and the other for Transient Analysis) showing the netlist and the graph clearly. Combine your images in a single folder and upload the folder as a zipped-file format to ninova.